



ECE 283 Lab3 Final Design Review

Mingjie Ma
Chengming Li

University of California, San Diego, La Jolla, CA, USA



Agenda

1. Project Background & Introduction
2. Test-Performance Overview
3. Chip Design Review in Cadence
4. Chip-Testing Review
5. Takeaway

Project Background & Introduction



UC San Diego



Project Background & Introduction

1. ECE266A - 9-bit high speed($F_s = 10\text{M Hz}$) SAR ADC
 1. Layout-focus Design
 1. Comparator, CDAC, Digital logic, Non-overlapping clock generator, switches
 2. Mega-Chip combinations
 1. 4 groups of chip into one BIG CHIP
 2. Dummy fill, seal ring, custom pads, custom-DeCaps, wavier submission
2. ECE266B – SAR ADC Testing
 1. PCB Design
 1. Mother(4-Layer) and daughterboard(2-Layer) combination
 2. Custom ADC chip footprint + Wirebonding Diagram
 2. Soldering & Assembly
 1. 0604 & 0802 Surface mount soldering
 3. Device characterization & Test - Automation
 1. Test Automation using Keysight instruments in Python
 2. Data processing and plotting in MatLab

Test - Performance Overview





Test - Specs Overview

Speces	Performance
$SNDR_{peak}$ @ 1kHz	50.23 dB
$SFDR_{peak}$ @ 1kHz	61.45 dB
SNR_{peak} @ 1kHz	50.68 dB
$THD_{2,peak}$ @ 1kHz	78.36 dB
$THD_{3,peak}$ @ 1kHz	61.45 dB


Chip Design Review in Cadence



UC San Diego



Comparator Remarks

 


- Symmetry layout in differential pair
- Achieved **90uV** offset in the differential pairs


Source Net	C+CC (F)	Difference(%)
FP(Hightlight)	9.8649f	
FN(Hightlight)	9.89668f	-0.32%
CP	6.76178f	
CN	6.68441f	1.144%
INP	5.42497f	
INN	5.40371f	0.39%



Comparator Layout

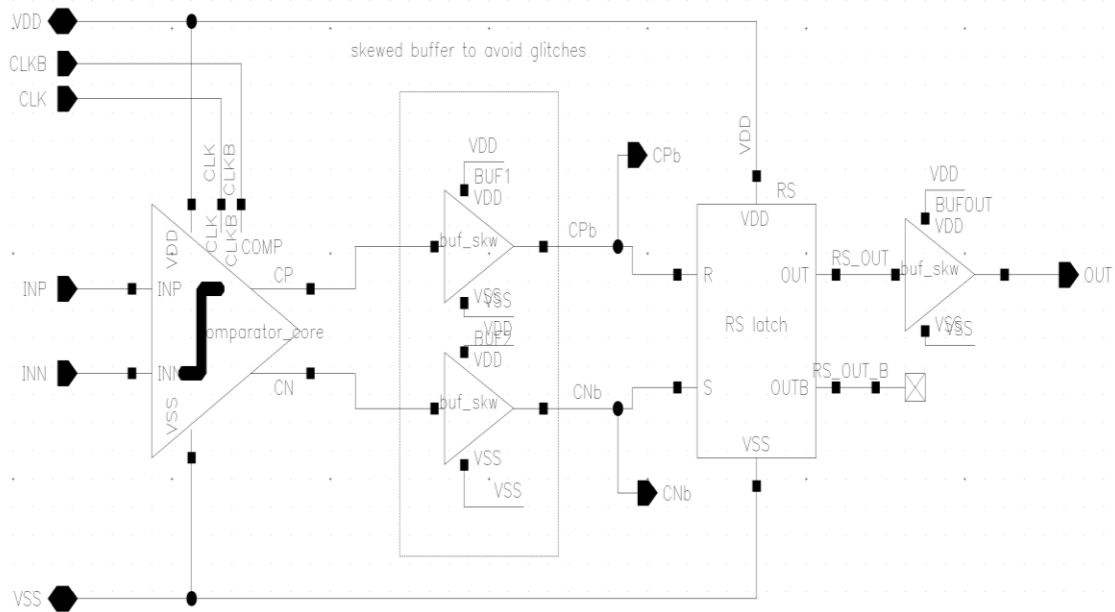

16.11u

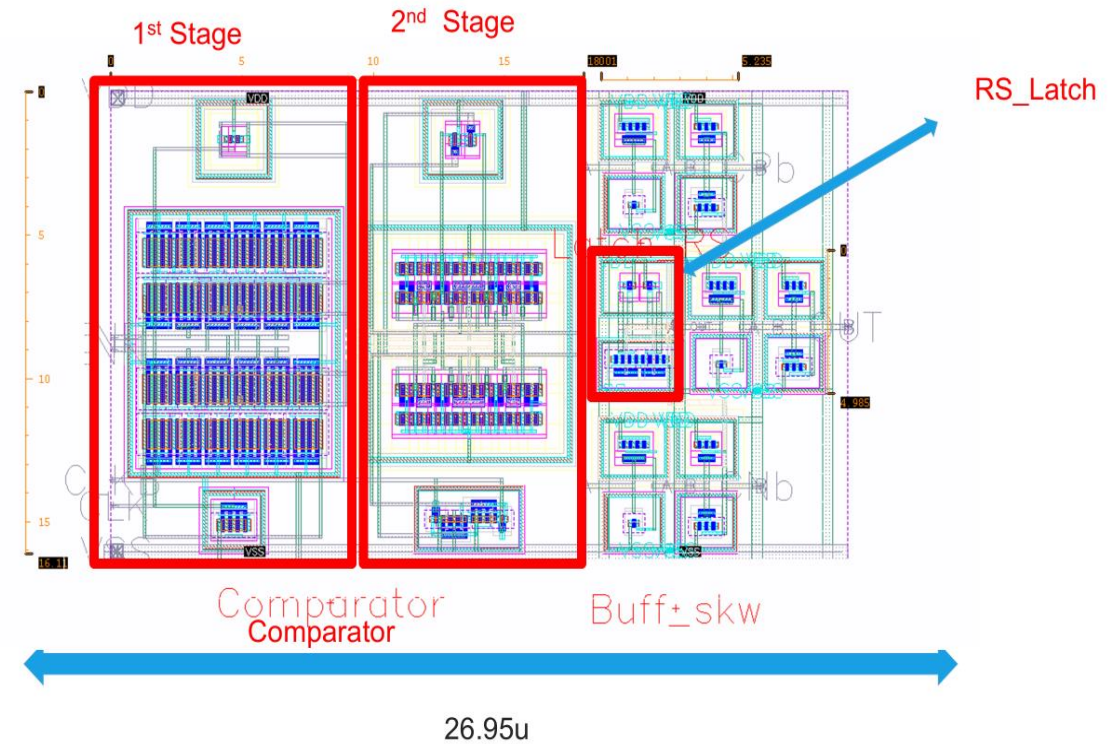





Custom unit Cap Remarks


Layer: M1 to M7 stack up

Size: 2.5u by 2.52u


CC: 5fF

  

2.52u

 

2.5u

 [illegible]



CDAC Remarks -2



Bit TopP	B0	B1	B2	B3	B4	B5	B6	B7	B8
CC(fF)	5.51874	11.0181	21.9972	44.1238	88.179	176.362	352.691	705.664	1413.44
Ratio		1.9996	3.9859	7.9952	15.9781	31.9569	63.9080	127.866	256.116

Bit TopN	B0	B1	B2	B3	B4	B5	B6	B7	B8
CC(fF)	5.51138	11.0222	21.9988	44.1662	88.2156	176.425	352.801	705.712	1413.26
Ratio		1.9998	3.9915	8.0136	16.0060	32.0110	64.0131	128.046	256.425




Final Layout – SAR-ADC

SE-DE-Nonoverlapping Generator

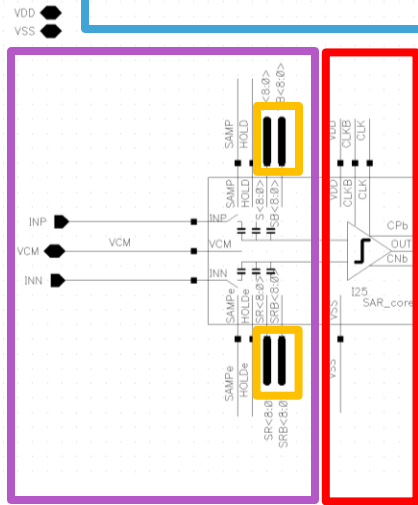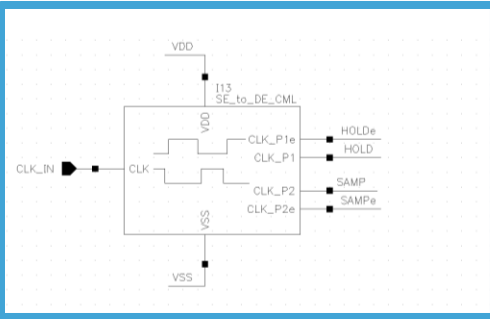


CDAC &
Switch Array

 


Comparator

SAR Digital Logic

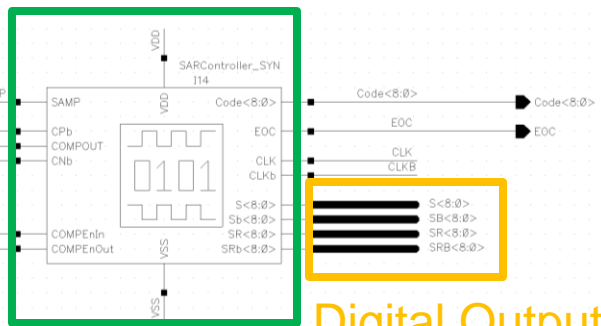

Digital Output


272.41u

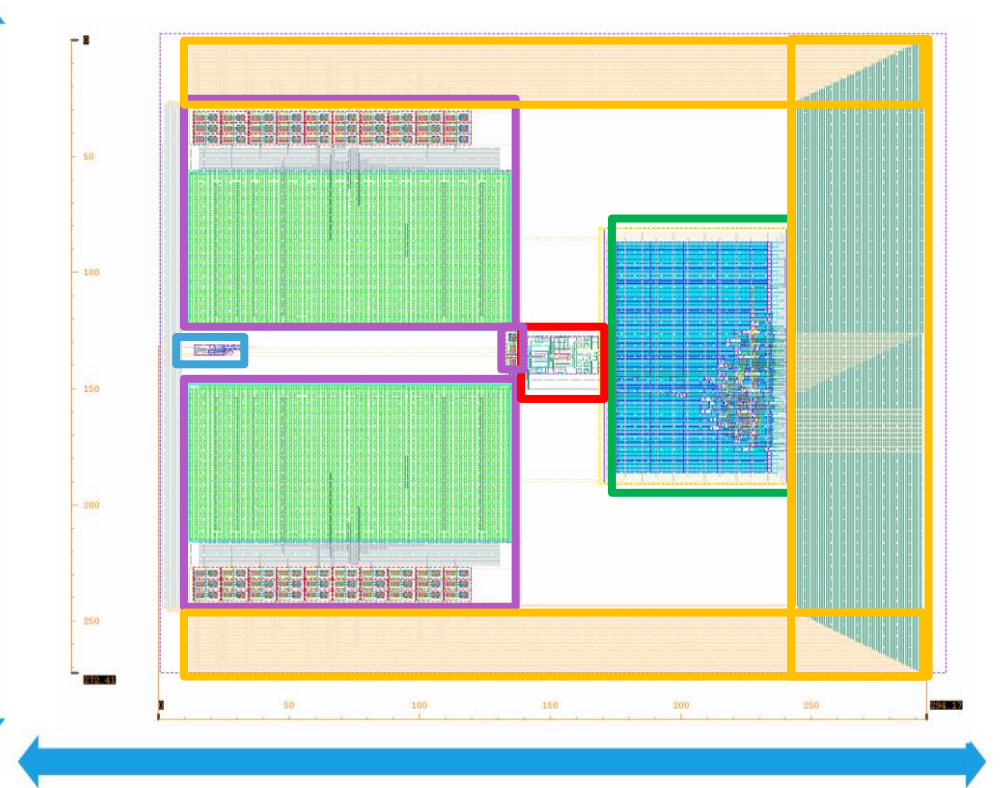


294.17u



Final Layout – SAR-ADC after Dummy Fill

 

Layout after dummy fill

 


Die Photo


SNR: 52.3 dB after
dummy fill



Mega Group 2 Chip Photos

 

Location of our
SAR Core

 


Chip-Testing Review




UC San Diego



MotherBoard BlockDiagram

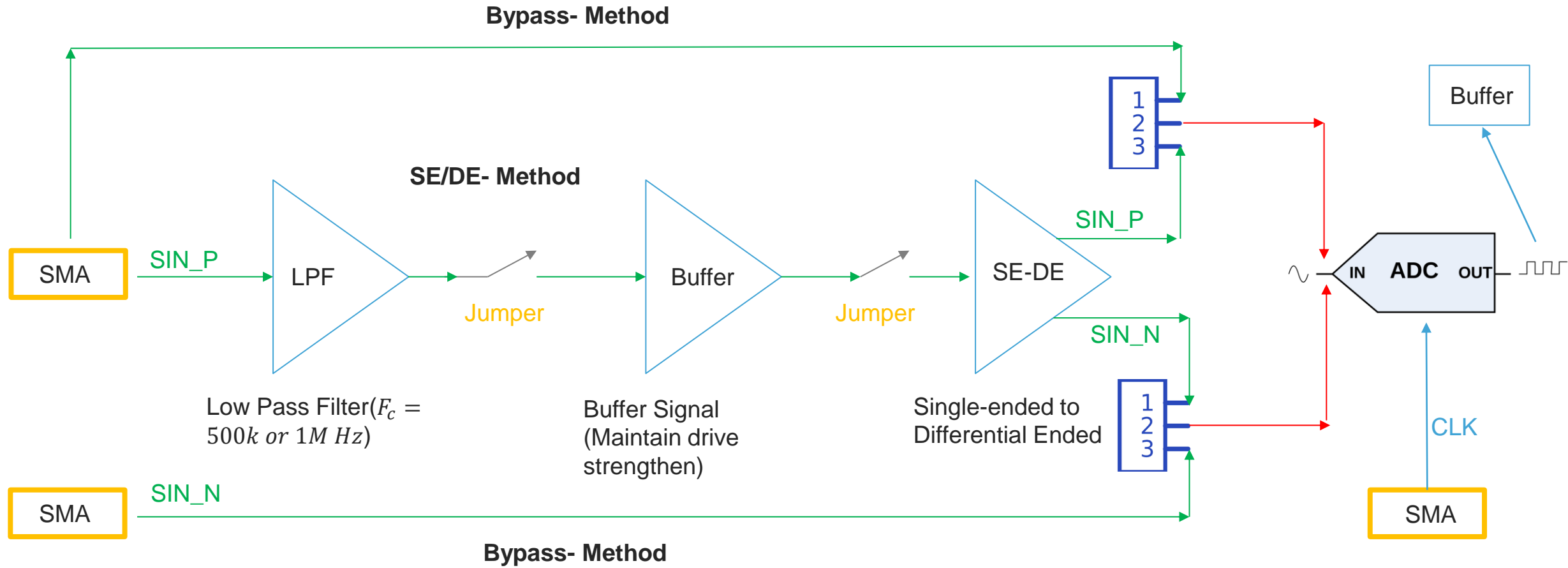


 


Chip Package and Wire bonding Diagram


Pin Number	Type	Description
1	Power	VDD_ESD
2	Power	VSS_ESD
3	Power	DVSS_T12
4	Power	VDD_T12
5	Digital Input	CLK_T12
6/7	Digital Input	MUX_SEL
8 - 16	Digital Output	ADC_RESULT
17	Digital Output	EOC
22/27/29/34/43/45/ 46/47/52	Power	AVSS
32	Analog Input	INN_T12
36/44	Power	VDD_ANA_ESD
38	Analog Input	VCM_T12
39	Analog Input	INP_T12



MotherBoard + DaugtherBoard 3D

  

MotherBoard + DaughterBoard

 

1. Modularized the Design

1. By having jumper between each IC
2. For debugging
3. SE-DE / ByPass Options

2. Testability

1. Jumper for GND for easy probing
2. Grab & Probe

3. Configurability

1. Potentiometer for tweaking the perfect Vcm, AVDD, AVDDESD

4. 4-Layer Stack

1. Signal
2. DGND + AGND
3. +5V
4. -5V



Board Bring-up Checklist

Power Supply Test					
Test No.	Test Plan	What Components	What Exepect to See	Status	Notes
0	Produce -5 V and 5 V on breadboard	Breadboard and Power supply with 3 separate power supply	Neg 5V and Pos 5V	Pass	
1	After connecting 2.5V, Measure the LDO U7 U8 U9's output	U7, U8, U9	1.5V @ Pin 5 of LDOS	Pass	
2	After connecting -5 V and 5V, make sure power vias are shown 5V and -5V correctly	3-Pins Jumer near the Vsin_IN_NP	Pos 5V on the leftmost pin and Neg 5V on the rightmost	Pass	
3	LDO U3 regulated down from 5V to 2.5	P1 Jumer Right Most Pin	2.5V on P1 rightmost	Pass	
4	LDO U11 regulated down from 2.5V to 0.5V	Jumer head in P1, U11's Pin 1 and 2, and TP	0.5V on TP	Pass	
5	Tweak Potentiometer U7 to get 1V for DVDD	Potentiometer near U7, Jumer Top pin	1V DVDD @ Jumer Top Pin	Pass	
6	Tweak Potentiometer U8 to get 1V for AVDDSD	Potentiometer near U8, Jumer Top pin	1V AVDD_ESD @Jumer Top Pin	Pass	
7	Tweak Potentiometer U9 to get 0.5V VCM	Potentiometer near U9, Jumer left pin	0.5V VCM @Jumper Left Pin	Pass	
Sig_IN Test					
0	Connect 200K Hz Offset 0V, Amp 0.4V Sine wave into J2 SM. J2 SMA, TestPoint Near J2		200K Hz Offset 0V, Amp 0.4V Sine wave	Pass	
1	U10(LPF) Connect to 1M filter choice 200K Hz Offset 0V, Amp 0.4V Sine wave shows up at P4, no distortion	U10 filter choice jumer, jumper head, P4 right pins, TP2	200K Hz Offset 0V, Amp 0.4V Sine wave into J2	Pass	
2	Connect P4 Jumer, signal go through U4 buffer and measure P12 Output	U4, P12 rightmost Pin	200K Hz Offset 0V, Amp 0.4V Sine wave	Pass	
3	U5(SE_DE) signal coming from P12, Measure SIN_IN_P and SIN_IN_N Sig property	P12 Jumer head SIN_IN_P header and SIN_IN_N header right most pin	SIN_P: 200K Hz Offset 0.5V, Amp 0.4V Sine wave SIN_N: 200K Hz Offset 0.5V, Amp 0.4V Sine wave, 180 out of phase	Pass	
Digital Test					
0	CLK Connect to J1	J1		Pass	
1	MUX Choice	Used female to female jumer to connect the MUX choices		Pass	MUX0: 1, MUX1: 0

1. By knowing what to expect after each IC
2. Actual vs. Expect
3. Handy to debug the problem



Test Setup Documentation

SE-DE Test Setup

1. Power Supply
 - a. 1 channel is used as 5V, 0.2A
 - b. 1 channel is used as -5V, 0.2A
 - c. 1 channel is used as 2.5V, 0.2A
2. Function Generator
 - a. SIN Input - Channel 1
 - i. High-Z Load
 - ii. 1Vpp
 - iii. 0 V offset
 - iv. Frequency at 1KHz as initial
 - b. Clock Input – Channel2
 - i. High-Z Load
 - ii. 2.5 Vpp
 - iii. 1.25 Offset
 - iv. Frequency at 1MHz
 - v. Duty Cycle 50%

c. Sync Both Channels every time the parameters are changed
3. Oscilloscope
 - a. Time Base 1ms/div
 - b. Digital Bus1
 - i. Digital Code 0-8 (C0-8)
 - ii. Digital Code 11 - End of Code (EOC)
 - iii. Trigger Level 1.8V
 - iv. Turns off Others
 - c. Trigger Source
 - i. EOC, D11 Rising Edge
 - ii. **Possibly CLK from Function Generator OR CLK from buffer**
 - d. Collect data
 - i. Stop or Single
 - ii. MSB First
 - iii. ASCII format
 - iv. Maximum Points


Bypass Setup

1. Power Supply
 - a. 1 channel is used as 5V, 0.2A
 - b. 1 channel is used as -5V, 0.2A
 - c. 1 channel is used as 2.5V, 0.2A
2. Function Generator
 - a. SIN Input - Channel 1
 - i. High-Z Load
 - ii. 1Vpp
 - iii. 0 V offset
 - iv. Frequency at 1KHz as initial
 - b. SIN Input Inverted - Channel 2
 - i. Polarity Inverted
 - ii. High-Z Load
 - iii. 1Vpp
 - iv. 0 V offset
 - v. Frequency at 1KHz as initial

c. Sync Both Channels every time the parameters are changed
3. Oscilloscope
 - a. WaveGen used as CLK
 - i. Load – Infinity
 - ii. Frequency – 1M
 - iii. Amplitude 2.5V
 - iv. Offset – 1.25V
 - v. Duty Cycle 50%
 - b. Time Base 1ms/div
 - c. Digital Bus1
 - i. Digital Code 0-8 (C0-8)
 - ii. Digital Code 11 - End of Code (EOC)
 - iii. Trigger Level 1.8V
 - iv. Turns off Others
 - d. Trigger Source
 - i. EOC, D11 Rising Edge
 - ii. Possibly CLK from Function Generator OR CLK from buffer
 - e. Collect data
 - i. Stop or Single
 - ii. MSB First
 - iii. ASCII format
 - iv. Maximum Points




Test Automation Setup - 1

 

1. Power Supply
 1. +5V, -5V, and 2.5V
2. Function Generator
 1. CLK & SIN INPUT
3. Oscilloscope
 1. Digital Analyzer
 2. Digital Output
4. 4-Layer Stack
 1. Signal
 2. DGND + AGND
 3. +5V
 4. -5V

Test Automation Setup - 2

 

1. Power Supply
 1. +5V, -5V, and 2.5V
2. Function Generator
 1. CLK & SIN INPUT
3. Oscilloscope
 1. Digital Analyzer
 2. Digital Output



Test Automation Code Prep

1. Keysight Connection Expert & Keysight Command Expert


1. Extremely **accelerate** the code development time
2. And check if the instrument is there

2. Python Test Automation

1. Function Generator
 1. 'Freq_coupling', 'FuncGenConnect', 'Load__setup', 'PWM_setup', 'Polarity_invert', 'Sin_setup', 'Sync_phase', 'UnitVpp_setup', 'Voltage_coupling', 'output_OFF', 'output_ON'
2. PowerSupply
 1. 'Channel_Select', 'Current_Setup', 'Output_OFF', 'Output_ON', 'PowerSupply_Connect', 'Voltage_Setup'
3. Oscilloscope
 1. 'DigitalDisplay_ON', 'Digitalizer_ON_OFF', 'Oscilloscope_Connect', 'Oscilloscope_RUN', 'Oscilloscope_SetBUS', 'Oscilloscope_Single', 'Oscilloscope_Stop', 'Oscilloscope_TimeBase', 'Oscilloscope_Trigger_Dchan', 'Oscilloscope_Trigger_External', 'Oscilloscope_WGen_Square', 'Oscilloscope_WGen_Square_OFF', 'Oscilloscope_WGen_Square_ON', 'Save_waveform', 'SetDigital_Threshold'


3. Code Version Control

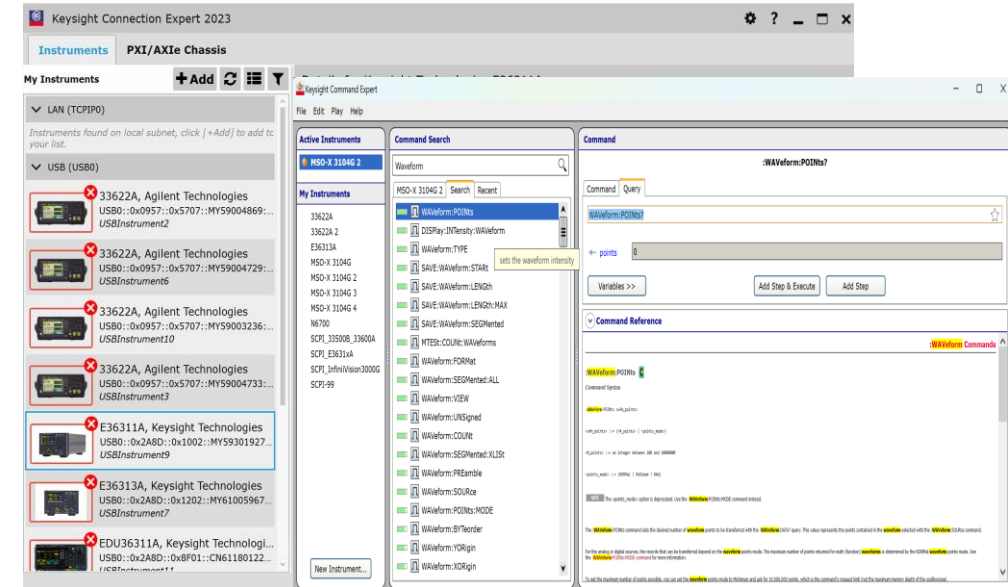1. GitHub
 1. **Never lost** what I did on “Yesterday”







Peak SNDR Plot

 

Speces	Performance
$SNDR_{peak}$ @ 1kHz	50.23 dB
$SFDR_{peak}$ @ 1kHz	61.45 dB
SNR_{peak} @ 1kHz	50.68 dB
$THD_{2,peak}$ @ 1kHz	78.36 dB
$THD_{3,peak}$ @ 1kHz	61.45 dB



INL & DNL Plot

 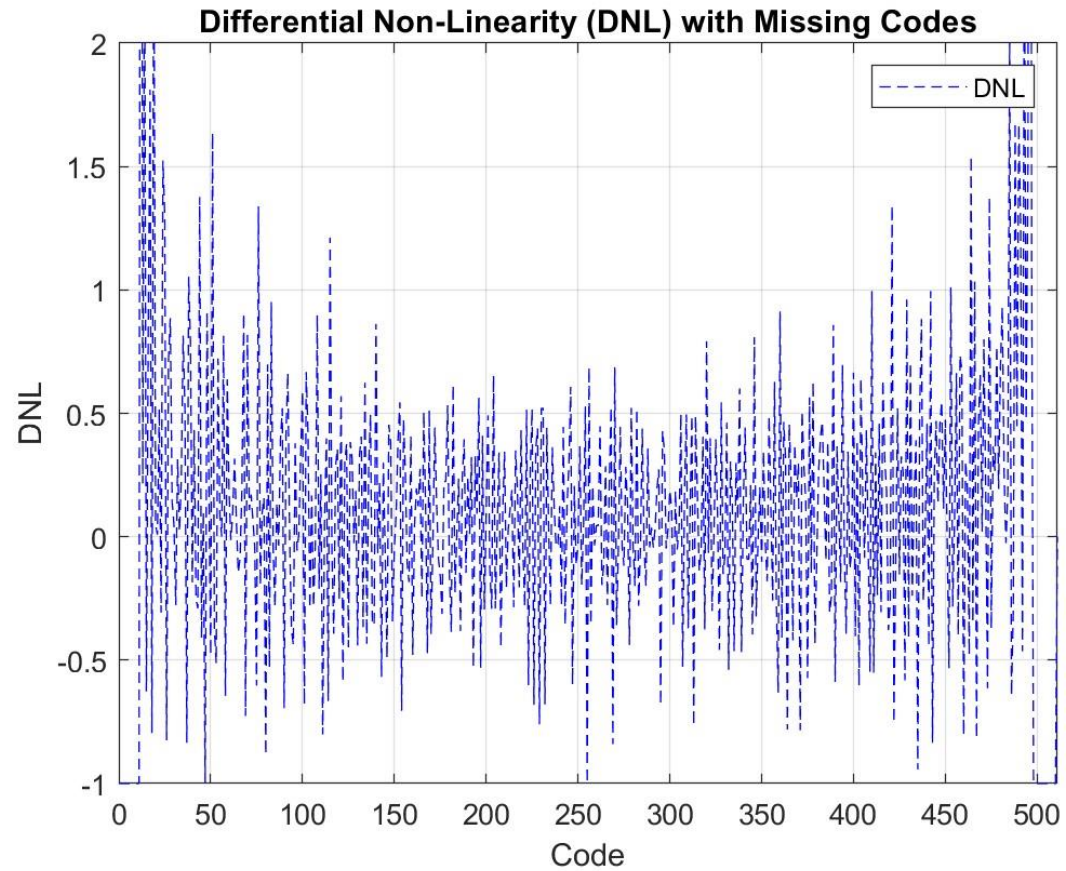



Future Work

1. **Improve** the code to make coherent sampling using: $\frac{f_{in}}{f_{sample}} = \frac{\# \text{ integer cycles}}{\# \text{ FFT_points}}$
 1. By adjusting the input frequency f_{in}
 2. By grabbing enough cycles, **no more no less (ideally prime number)**
 3. By grabbing **2^x** data points
2. **Rework** the mother and daughter board
 1. Putting more decaps to **filter-out the supply noise**
 2. Make it to be plugging-in and **direct-use Eval-Board**
3. **Bypass** the fronted-end module

Takeaway



UC San Diego



Takeaway

1. Always Always Always **document everything**
2. Simple Eval-board Design = Robust **Debuggability & Reconfigurability**
3. **Cross-check** everything with partners



Acknowledgement

- Prof. Hall
 - For running this 6-months course/projects
 - Helping us debug the problems
- TA: Darshan
 - Supporting the Lab work
 - Extending the Lab Hours
- MegaGroup2
 - Putting everything together in the Mega-Chip
- Apple
 - For sponsoring this projects, buying the chips, PCBs, components, etc
- Keysight
 - Instruments, instrument command & connection expert