





ECE 266 Lab3 Design Review

Mingjie Ma
Chengming Li

University of California, San Diego, La Jolla, CA, USA




CC: 5fF

  



Schematic-singleDAC(cap bank)

Dummy

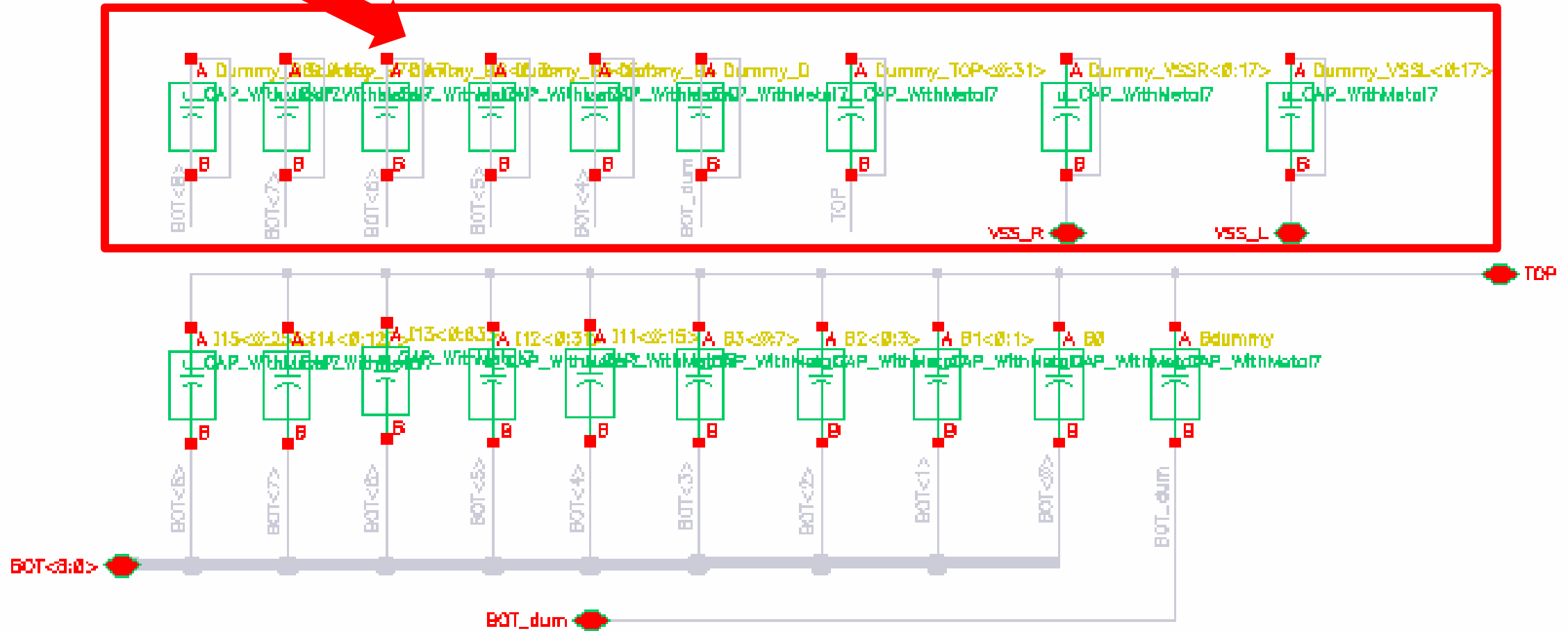



Metal Width vs. Current

- How much current we need?
 - $Q = CV$
 - $\frac{dQ}{dt} = I = C \times \frac{dV}{dt}$
 - $\int I dt = \int C dV$
 - $I \Delta t = C \times VDD$
 - $I(\text{per unit Cap}) = \frac{C \times VDD}{\Delta t} = \frac{5fF \times 1}{1.65\mu s} = 3n A$
 - $I(\text{per column}) = 3n * 16 = 48n A$
- How wide of the trace should be?(Read from PDK doc)
 - M1(0.4um): 0.57 mA
 - M2 – M7 (0.4um): 0.72 mA
 - M2 – M8 (0.8um): 1.47 mA



Bit	B0	B1	B2	B3	B4					
CC(fF)	10.14	21.8	44.04	58.25	101.5					
Ratio		2.145	2.02	1.322	1.74					



singleDAC(cap bank) Floorplan

D_VSS	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	2	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	2	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	2	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	1	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	1	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	0	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	D	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	D_8	D_8	D_8	D_8	D_8	D_8	D_8	D_8	D_7	D_7	D_7	D_7	D_6	D_6	D_5	D_5	D	D_4	D_6	D_6	D_7	D_7	D_7	D_7	D_8	D_8	D_8	D_8	D_8	D_8	D_8	D_8	D_VSS

Bit	B0	B1	B2	B3	B4					
C+CC(f F)	6.4994	12.333	23.683	45.248	86.676					
Ratio		1.898	1.920	1.910	1.916					



RCX Cap Table

No.	Layout Net	Source Net	C Total (F)	CC Total (F)	C+CC Total (F)
1	BOT<0>	BOT<0>	1.02960E-15	6.79001E-15	7.81962E-15
2	BOT<1>	BOT<1>	1.59393E-15	1.27679E-14	1.43618E-14
3	BOT<2>	BOT<2>	2.93767E-15	2.58180E-14	2.87557E-14
4	BOT<3>	BOT<3>	5.43015E-15	5.11647E-14	5.65949E-14
5	BOT<4>	BOT<4>	1.09642E-14	9.56543E-14	1.06618E-13
6	BOT<5>	BOT<5>	2.15877E-14	1.88712E-13	2.10300E-13
7	BOT<6>	BOT<6>	4.38039E-14	3.69387E-13	4.13191E-13
8	BOT<7>	BOT<7>	8.65712E-14	7.25979E-13	8.12550E-13
9	BOT<8>	BOT<8>	1.70076E-13	1.40478E-12	1.57486E-12
10	BOT_dum	BOT_DUM	2.35177E-15	7.57801E-15	9.92978E-15
11	TOP	TOP	2.99117E-13	2.73160E-12	3.03072E-12
12	VSS_L	VSS_L	2.11706E-14	3.46606E-15	2.46367E-14
13	VSS_R	VSS_R	2.11610E-14	3.47787E-15	2.46389E-14

Find Nets:				Coupling to: <input checked="" type="radio"/> All Nets <input type="radio"/> Specified Nets	
BOT<6> BOT<7> *					
Type	Count	Total	Source	Layout Net: BOT<7> Source Net: BOT<7> Capacitors: C (1 C, C=8.65712E-14)	
C	1	8.65712E-14		No.	Value (F)
CC	9	7.25979E-13		1	8.65712E-14
CC BOT<0>	1	6.03087E-17	BOT<0>		
CC BOT_dum	1	4.69659E-16	BOT_DUM		
CC BOT<2>	1	8.18673E-16	BOT<2>		
CC BOT<3>	1	1.14413E-15	BOT<3>		
CC BOT<4>	1	2.47462E-15	BOT<4>		
CC BOT<5>	1	4.49197E-15	BOT<5>		
CC BOT<6>	1	9.23773E-15	BOT<6>		
CC BOT<8>	1	2.77877E-14	BOT<8>		
CC TOP	1	6.79494E-13	TOP		

Example:

Bot7

C: 86.5f F

CC:

1)Top 679.49f F


2)Bot6: 27.7 f F



Layout - singleDAC – Bit0123 - center

Non-symmetry
Bit 0:3 (M1, M3, M5, M7) overlapping

76.74u

 


 121.97u



- Symmetry
- Less CC between Bits and
- Less CC effects to the Dummy for bit0

- Sensitive to C(w.r.t substrate)
- Sensitive to the length of Bit 0:3
- Non-binary routing






Layout - singleDAC – Robust C+CC

Improvement:

- Higher metal used for M0:3
- Binary routing
- Robust C+CC sensitivity

76.74u

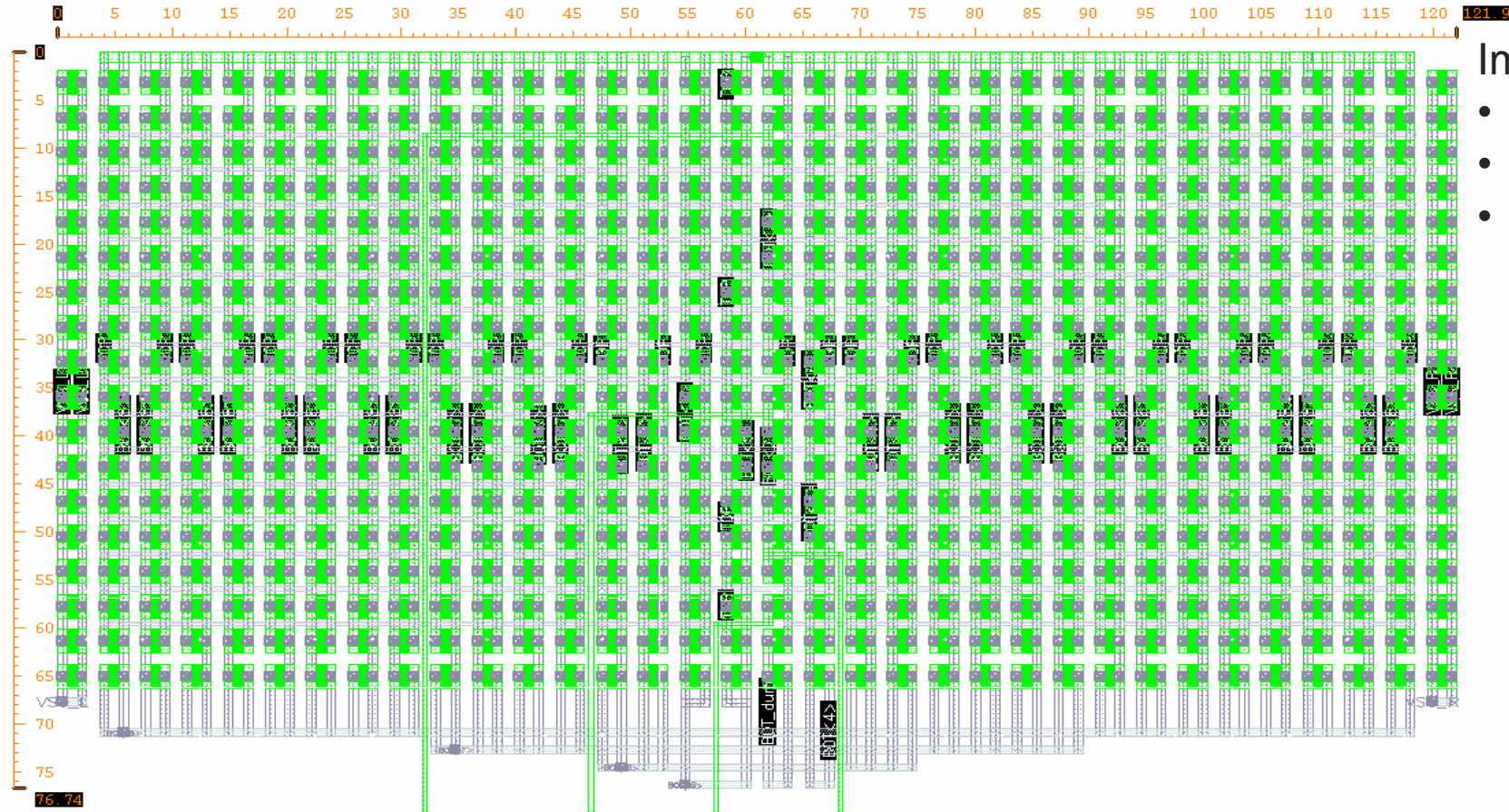

121.97u



RCX Cap Table

Bit	B0	B1	B2	B3	B4	B5	B6	B7	B8
C+CC(f F)	7.819	14.36	28.755	56.594	106.62	210.30	413.19	812.55	1574.86
Ratio		1.84	2.00	1.97	1.88	1.97	1.96	1.97	1.94



Appendix – Old Version uCap

