

ECE266 Lab4


Chengming Li, Mingjie Ma

PID A59026442, A69028795

Email: chl248@ucsd.edu


mim029@ucsd.edu

Top Level Schematic

 


Top Schematic

Schematic of Pad Ring

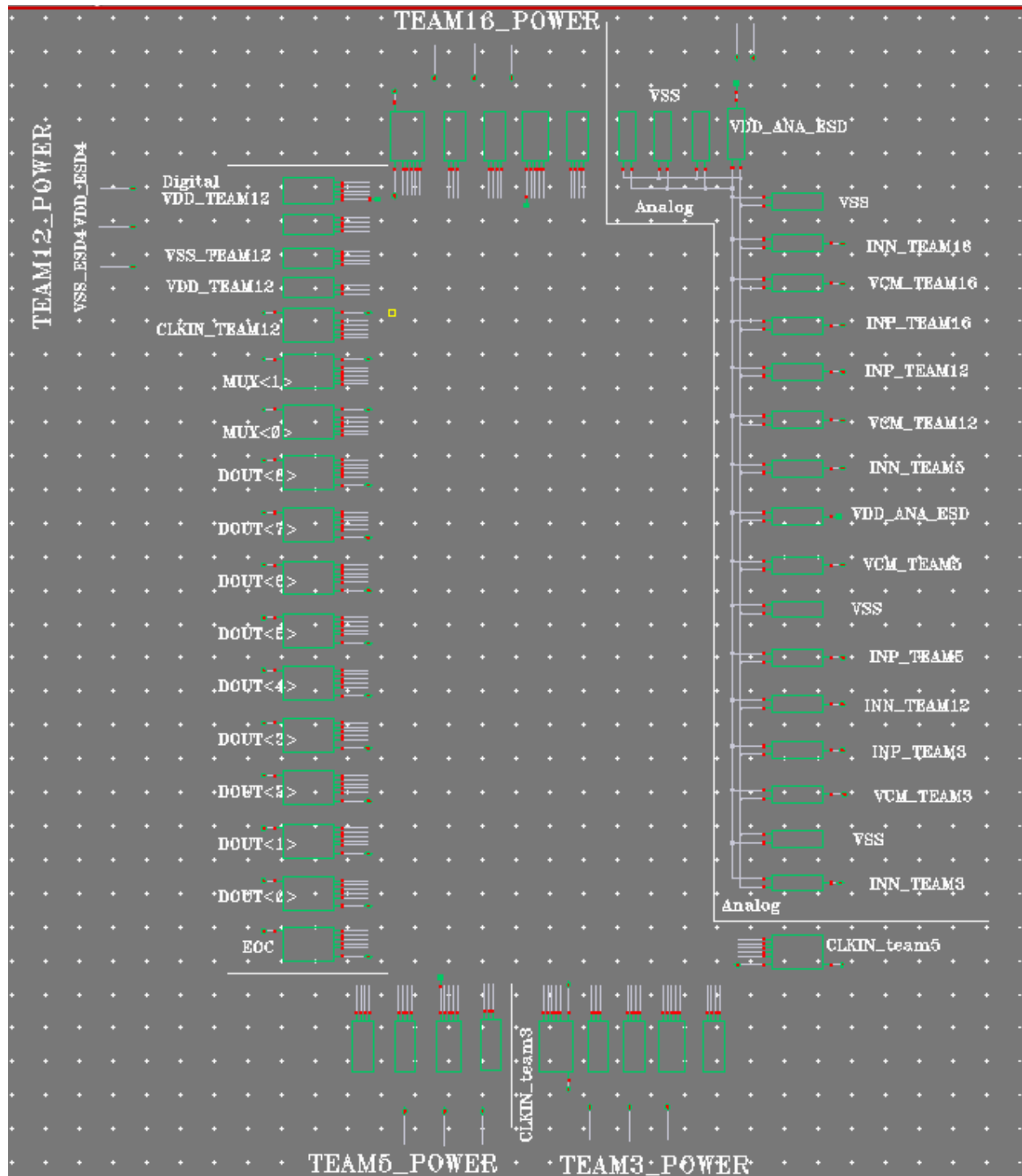

Pad Ring Schematic

Picture of Top-level Layout

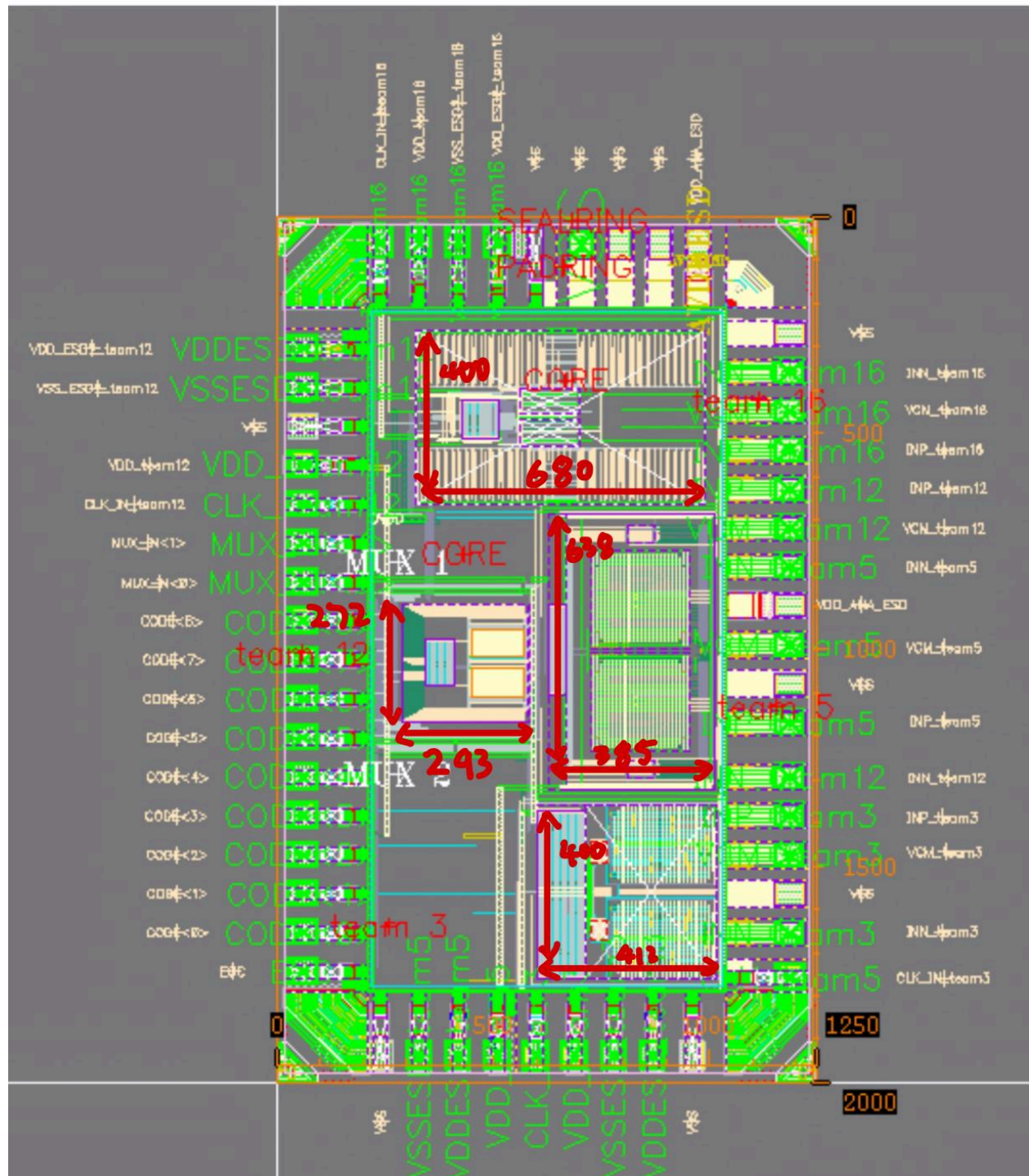

Top Level Layout (294.17 * 272.41)

DRC Result Summary

Calibre - RVE v2019.4_36.18 : Top.drc.results

File View Highlight Tools Window Setup Help

Filter: Show All Top, 25920 Results (in 69 of 73 Checks)

Check / Cell	Results	Flat
Check M1.DN.1	6	6
Check M1.DN.4	2	2
Check M2.DN.1	6	6
Check M2.DN.4	1	1
Check M3.DN.1	6	6
Check M3.DN.4	1	1
Check M4.DN.1	6	6
Check M4.DN.4	2	2
Check M7.DN.1	6	6
Check M7.DN.4	2	2
Check M8.DN.1	7	7
Check M8.DN.4	1	1
Check M9.DN.2	4	4
Check RM.WARN.4.M5	91	31890
Check RM.WARN.4.M6	36	42768
Check ESD.22g	64	1024
Check RR.AR.SP.PO.S.2	65	1453
Check RR.AR.SP.PO.EX.2	259	20316
Check RR.AR.SP.PO.S.5	216	6170
Check RR.AR.SP.PO.S.14	1000	5757
Check RR.RE.SP.PO.EN.1	1000	5635
Check RR.RE.SP.PO.EN.2	77	1435
Check RR.AR.SP.PO.EN.3	105	426
Check RR.RE.SP.O.S.11	1000	1589

M1.DN.1 (6 M1 local density must be >= 0.1 range over 75 um x 75 um step 37.5 um)

M1 CHECK = M1: NOT MIDNILL_EXO

CHIP_CHECK = CHIP NOT MIDNILL_EXO

ERR_WIN = DENSITY M1_CHECK (CHIP_CHECK < M1_DN_1L_WINDOW M1_DN_1L_W STEP M1_DN_1L_S INSIDE OF LAYER CHIP: BACKUP

[AREA(M1_CHECK)/AREA(CHIP_CHECK)]

P = WITH WIDTH (ERR_WIN NOT MIDNILL_EXO) >= M1_DN_1L_W


Check M1.DN.1

Note: Our mega group2 is thinking of waiving M2-M9. This is the DRC result before we fill out the M1 Metal.(Deadline of this report is 5PM Fri 07/06). At this time stamp, we still have 1 group that didn't finish their M1 local dummy fill. So the M1 DN is still shown in the above.

Ideally, the M1 DN error will be gone. And M2-M9 DN are expected to be there.

RR Errors are ignored in the layout

ANT Summary

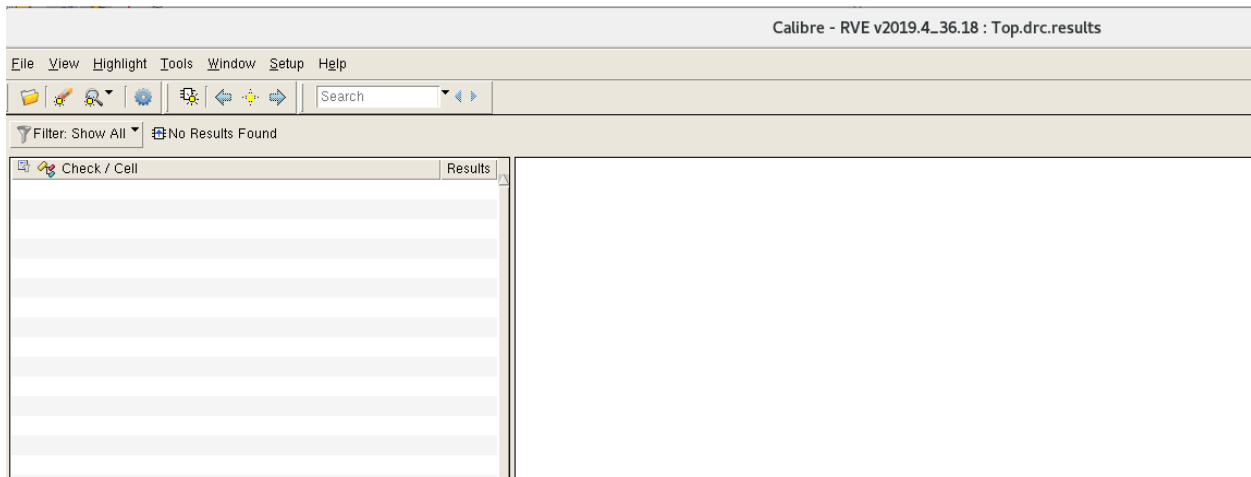

LVS Result Summary

Calibre - RVE v2019.4_36.18 : svdb Top

Window Setup Help

Search

Extraction Results Comparison Results

Layout Cell / Type	Source Cell	Nets	Instances	Ports
Top	Top	10188L, 10188S	18272L, 18272S	42L, 42S

Cell Top Summary (Clean)

CELL COMPARISON RESULTS (TOP LEVEL)

#

CORRECT #

#####


✓
✓
✓
✓
✓

Warning: Unbalanced smashed mosfets were matched.
Warning: Ambiguity points were found and resolved arbitrarily.

LAYOUT CELL NAME: Top
SOURCE CELL NAME: Top


8

Top-level simulation with pin-model

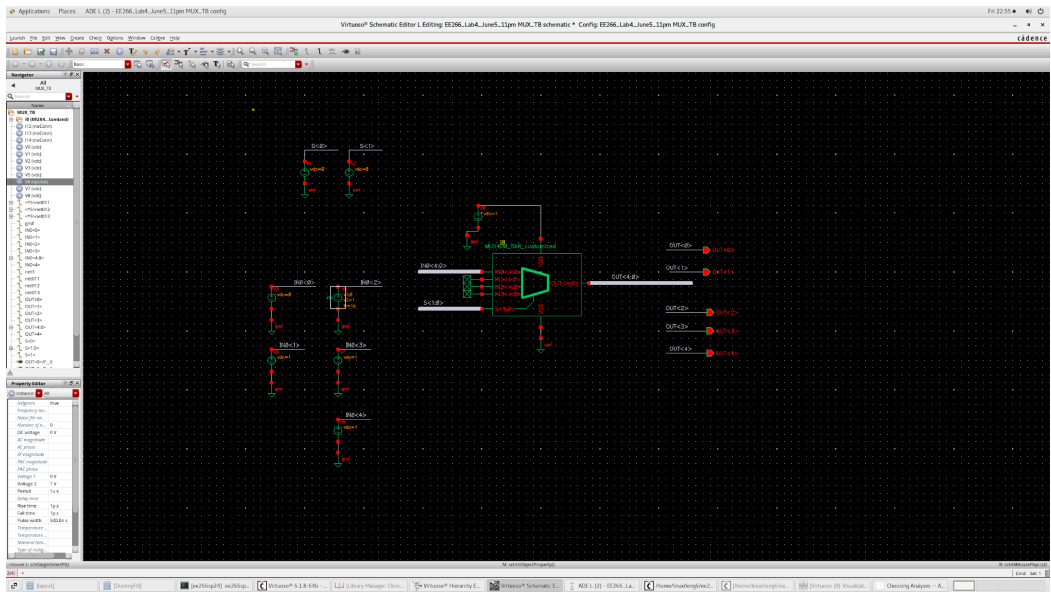


DC Response

Name		bit
/IN0<4:0>		
<div><div></div><div>/IN0<4></div></div>	<div><div></div><div></div></div>	/IN0<4>
<div><div></div><div>/IN0<3></div></div>	<div><div></div><div></div></div>	/IN0<3>
<div><div></div><div>/IN0<2></div></div>	<div><div></div><div></div></div>	/IN0<2>
<div><div></div><div>/IN0<1></div></div>	<div><div></div><div></div></div>	/IN0<1>
<div><div></div><div>/IN0<0></div></div>	<div><div></div><div></div></div>	/IN0<0>
/OUT<4:0>		
<div><div></div><div>/OUT<4></div></div>	<div><div></div><div></div></div>	/OUT<4>
<div><div></div><div>/OUT<3></div></div>	<div><div></div><div></div></div>	/OUT<3>
<div><div></div><div>/OUT<2></div></div>	<div><div></div><div></div></div>	/OUT<2>
<div><div></div><div>/OUT<1></div></div>	<div><div></div><div></div></div>	/OUT<1>
<div><div></div><div>/OUT<0></div></div>	<div><div></div><div></div></div>	/OUT<0>

 

MUX TB Circuit

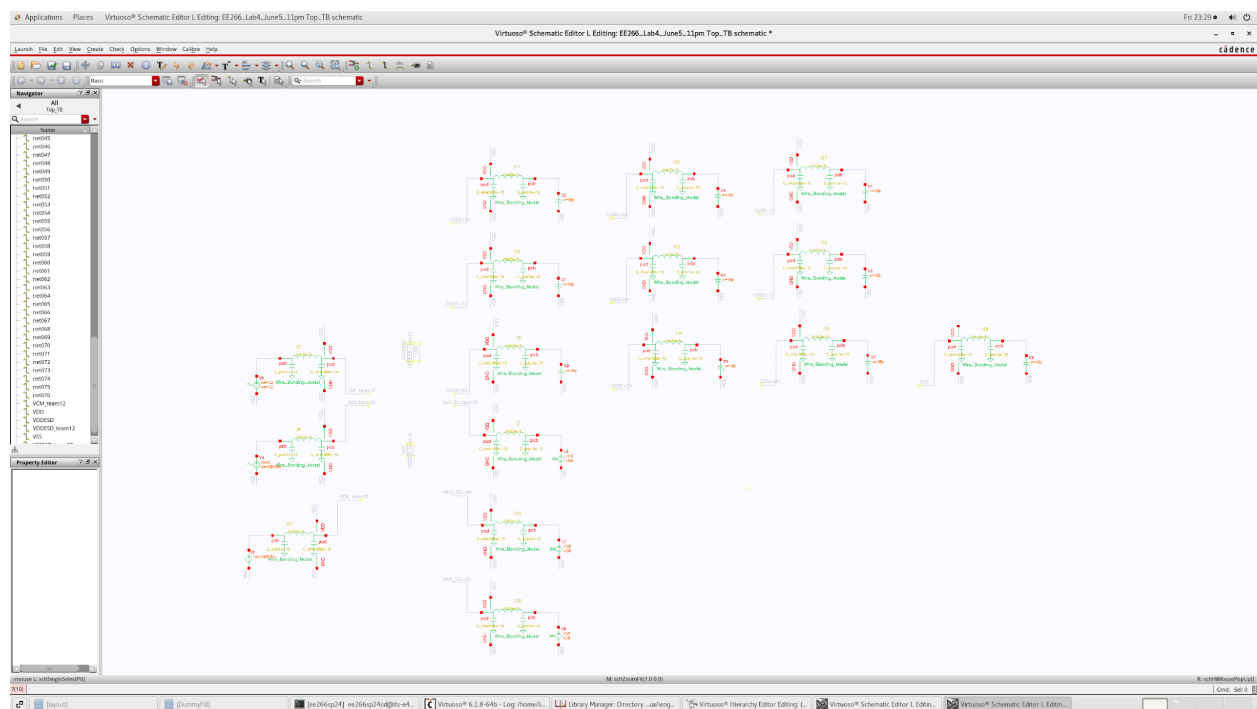

Top Level TB schematic

Comments and conclusions


1. Conclusions

- a. Mega group2 divided up the work into padring, seal ring, core level, floorplanning, top level routing, decap, mixer, buffer, and dummy filling
- b. We started developing the work from top to bottom, and cleaned the drc and lvs at each level. So at the top level, the DRC and LVS were much easier to resolve.
- c. Our sub-group is responsible for padring connections, decap design and routing, seal ring design, and waiver presentation preparation.
- d. For padring connection, we realized how different it is between the analog pad and digital pad. And how the pad will be powered through the pad ring. This is a very good experience learning the mechanism of IO Pad
- e. For Decap design, we use a very wide and thick gate oxide transistor-capacitor with $w=10u$ and $l = 10u$. The decap filling helps a lot in solving the Density problem in M1 and M2.
- f. Seal ring, we know how to build a mosaic and how the delta x and y can be tweaked to fulfill the requirement. Originally there are some overlapping DRC, and we were able to fix it by tweaking the #of mosaic and delta x to fix it
- g. This is our group's first time preparing the waiver presentation slices. It is a good learning experience to understand why and how we need this. It's good preparation for the future tape out.

2. Something I learned from this lab are:

- a. The design methodology needs to be from top to bottom, which makes it easier to route and clean drc and lvs errors.
- b. The mechanism of IO Pads. And how to customize the pad ring for our circuit specific use.
- c. Creating Decap will be useful for both circuit-purpose as reducing IO drop in the rails and Density-error purpose.
- d. Understanding the need and purpose of Seal rings during chip manufacturing.
- e. How to do dummy filling and using a dummy exclusion layer in the layout.
- f. Waiver presentation slices.
- g. Streaming in and back the gds file with dummy filling.
- h. How dummy filling affect the ratio of Capacitor DAC
- i. Team work

Appendix

 

Customized 10u Decap