




ECE 283 Lab1 Design Review

Mingjie Ma
Chengming Li

University of California, San Diego, La Jolla, CA, USA


Chip Package and Wire bonding Diagram

 

Pin Number	Type	Description
1	Power	VDD_ESD
2	Power	VSS_ESD
3	Power	DVSS_T12
4	Power	VDD_T12
5	Digital Input	CLK_T12
6/7	Digital Input	MUX_SEL
8 - 16	Digital Output	ADC_RESULT
17	Digital Output	EOC
19/34/43/45/46/47	Power	AVSS
32	Analog Input	INN_T12
36/44	Power	VDD_ANA_ESD
38	Analog Input	VCM_T12
39	Analog Input	INP_T12





DaughterBoard Layout

 




DaughterBoard Layout

  



DaughterBoard 3D View

 

Top Layer: Signal Only

Bottom Layer: 3 VSS

Decap: 100nF and 1 uF, 0805


Try to put them as close as possible to the IC VDDs

Header: 100 mil pitch, but there is a danger of mismatching the position in the motherboard.

Solution: Record the coordinates of each corner of each header



Schematic - motherboard

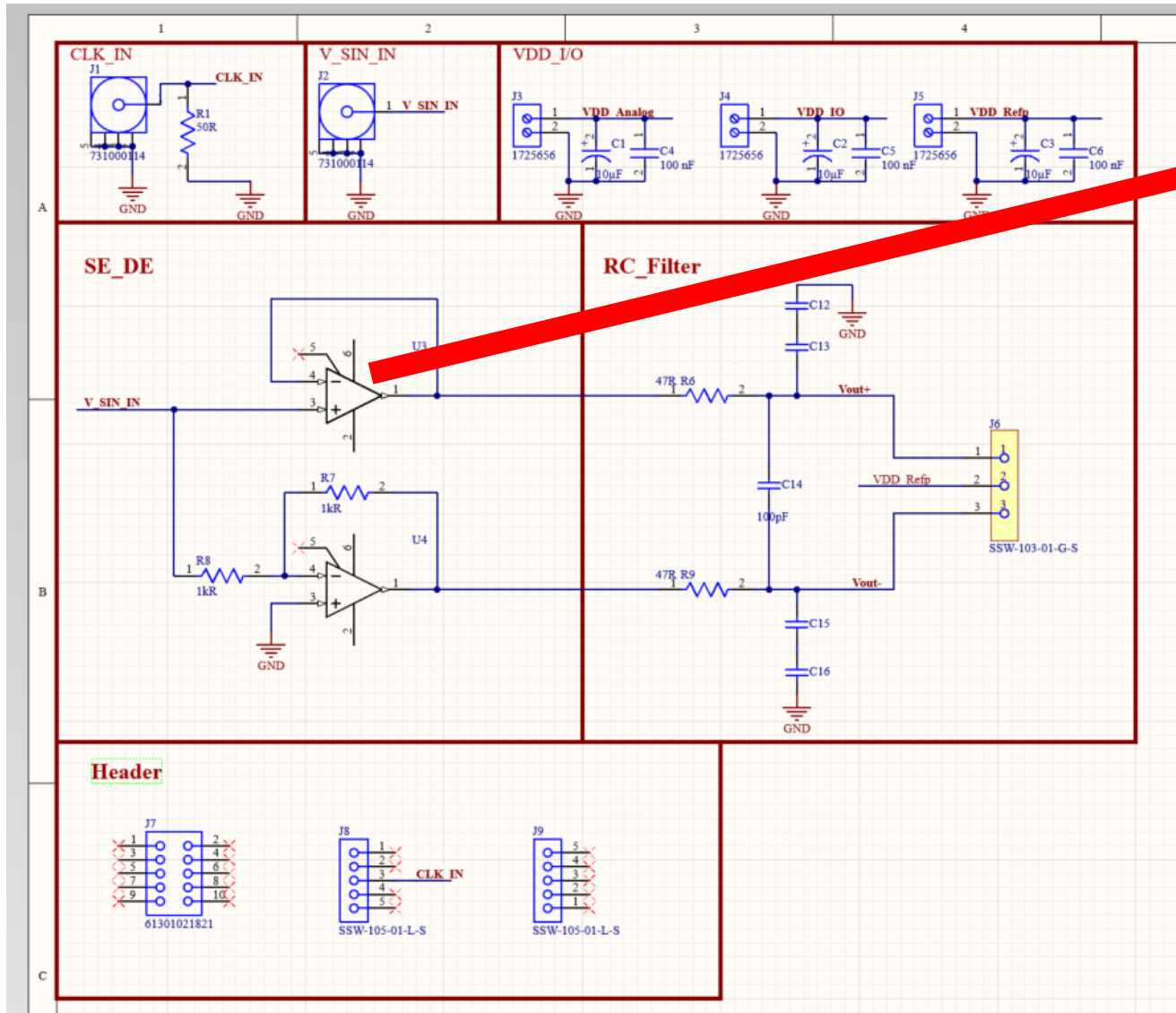


Opamp: LMH6611MKENOPB

- Gain Bandwidth Product - 135 MHz
 - -3db Bandwidth - 365 MHz
 - Voltage - Input Offset 74 μ V
 - CMRR - min 79dB, typ 98 dB
 - PSRR – min 81dB, typ 96 dB
-
- Question: what other specs should I consider in terms of linearity?



LTspice – SE-DE Simulation

 


SEDE Output after RC filter

- V_p – 1.2V (1.8V input)
 - R_{filter} – 47 ohm
 - $C_{\text{filter to gnd}}$: 0.5nF
 - $C_{\text{filter_common}}$: 0.1nF
-
- Question: should we worry about the attenuation?



LTspice – SE-DE Simulation

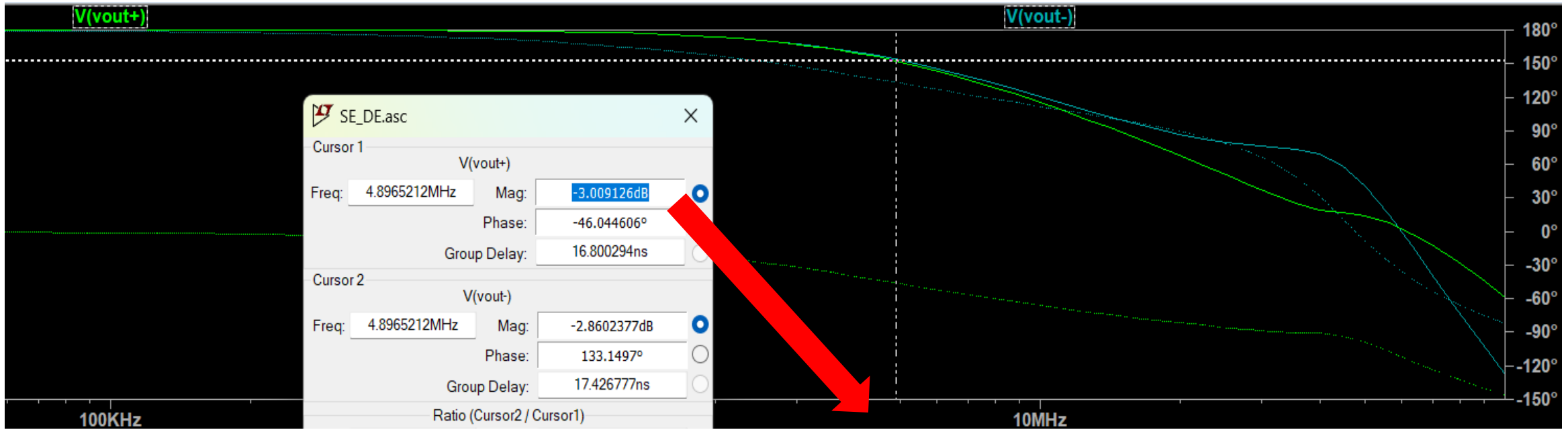

SEDE AC Output


- -3dB at 4.89MHz

- Question: is this ok?



MotherBoard Layout

3900mil

 


3000mil

Not finished yet



MotherBoard 3D View

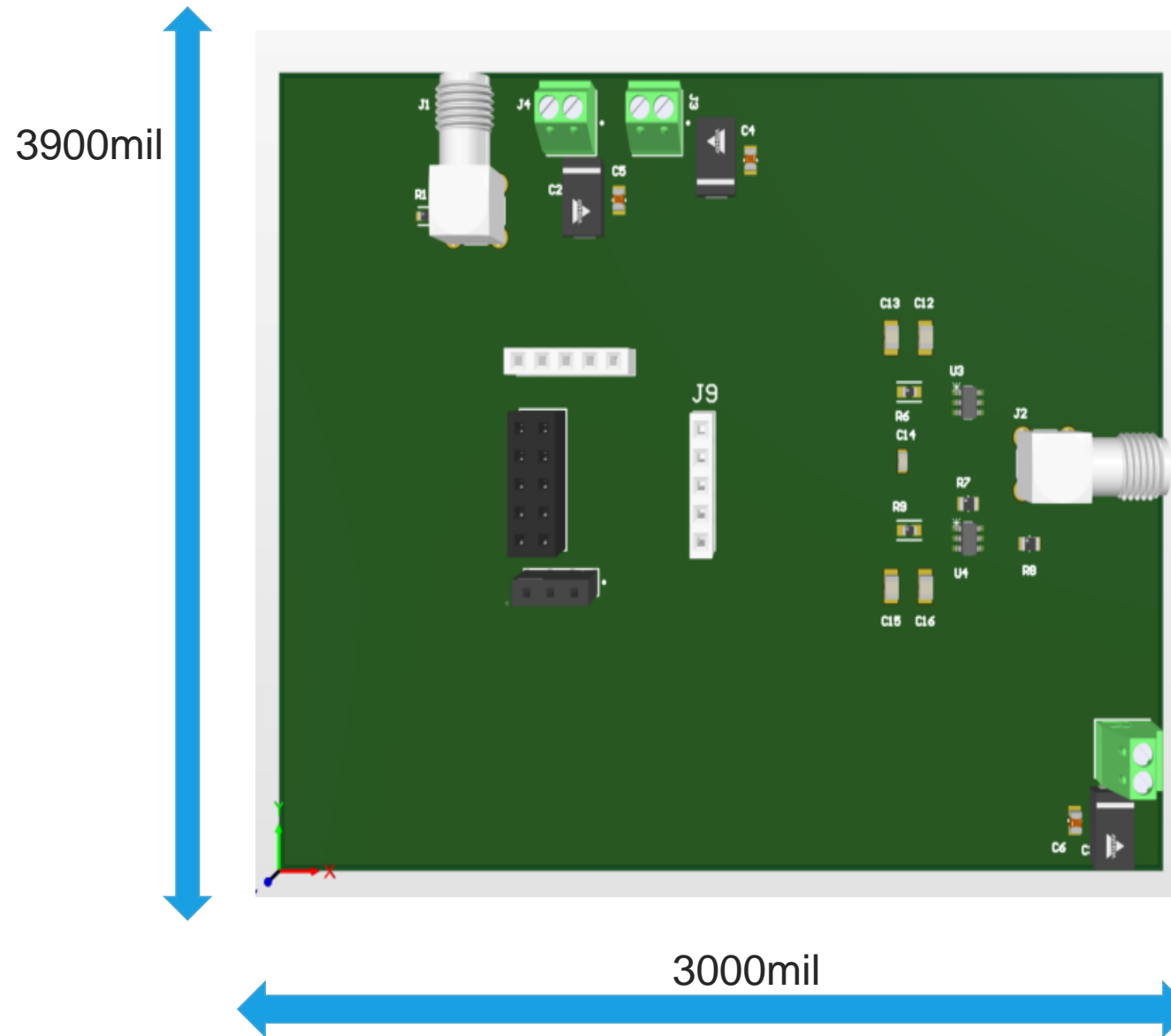

Not finished yet



Q & A