



ECE 266 Lab3 Design Review

Mingjie Ma
Chengming Li

University of California, San Diego, La Jolla, CA, USA





uCAP Layout


Layer: M1 to M7 stack up

Size: 2.5u by 2.52u

CC: 5fF

  

2.52u

 


2.5u



Schematic-singleDAC(cap bank)

Dummy

 



Metal Width vs. Current

- How much current we need?
 - $Q = CV$
 - $\frac{dQ}{dt} = I = C \times \frac{dV}{dt}$
 - $\int I dt = \int C dV$
 - $I \Delta t = C \times VDD$
 - $I(\text{per unit Cap}) = \frac{C \times VDD}{\Delta t} = \frac{5fF \times 1}{1.65\mu s} = 3n A$
 - $I(\text{per column}) = 3n * 16 = 48n A$
- How wide of the trace should be?(Read from PDK doc)
 - M1(0.4 μ m): 0.57 mA
 - M2 – M7 (0.4 μ m): 0.72 mA
 - M2 – M8 (0.8 μ m): 1.47 mA



Bit	B0	B1	B2	B3	B4					
CC(fF)	10.14	21.8	44.04	58.25	101.5					
Ratio		2.145	2.02	1.322	1.74					


- The ratio doesn't match, the floorplan is not used



Layout Iteration1 - singleDAC – Bit0123 - center

Non-symmetry
Bit 0:3 (M1, M3, M5, M7) overlapping

76.74u

 


 121.97u



- Symmetry
- Less CC between Bits and
- Less CC effects to the Dummy for bit0

- Sensitive to C(w.r.t substrate)
- Sensitive to the length of Bit 0:3
- Non-binary routing






Final singleDAC(cap bank) Floorplan

D_VSS	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_Top	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	3	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	2	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	2	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	2	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	1	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	1	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	0	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	8	8	8	8	8	8	8	8	7	7	7	7	6	6	5	5	D	4	6	6	7	7	7	7	8	8	8	8	8	8	8	8	D_VSS
D_VSS	D_8	D_8	D_8	D_8	D_8	D_8	D_8	D_8	D_7	D_7	D_7	D_7	D_6	D_6	D_5	D_5	D	D_4	D_6	D_6	D_7	D_7	D_7	D_7	D_8	D_8	D_8	D_8	D_8	D_8	D_8	D_8	D_VSS

Bit	B0	B1	B2	B3	B4	B5	B6	B7	B8
CC(fF)	5.4927	10.985	21.970	43.944	87.885	175.77	351.53	703.08	1406.1
Ratio		2	3.9999	8.000	16.000	32.000	63.999	128.00	256.00

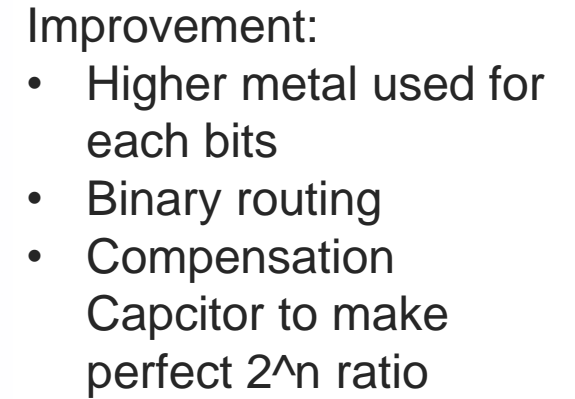

- Improvement:
- Higher metal used for each bits
 - Binary routing
 - Compensation Capacitor to make perfect 2^n ratio



CDAC RCX Cap Table

Bit TopP	B0	B1	B2	B3	B4	B5	B6	B7	B8
CC(fF)	5.51874	11.0181	21.9972	44.1238	88.179	176.362	352.691	705.664	1413.44
Ratio		1.9996	3.9859	7.9952	15.9781	31.9569	63.9080	127.866	256.116

Bit TopN	B0	B1	B2	B3	B4	B5	B6	B7	B8
CC(fF)	5.51138	11.0222	21.9988	44.1662	88.2156	176.425	352.801	705.712	1413.26
Ratio		1.9998	3.9915	8.0136	16.0060	32.0110	64.0131	128.046	256.425




SAR-Core RCX Cap Table

Bit TopP	B0	B1	B2	B3	B4	B5	B6	B7	B8
CC(fF)	5.51874	11.0182	21.9978	44.0338	88.082	176.21	352.332	705.239	1413.18
Ratio		1.9965	3.9860	7.9789	15.9605	31.9293	63.8428	127.789	256.069

Bit TopN	B0	B1	B2	B3	B4	B5	B6	B7	B8
CC(fF)	5.51137	11.0222	21.9987	44.0749	88.1173	176.271	352.44	705.293	1413.41
Ratio		1.9999	3.9915	7.997	16.0060	31.9831	63.9478	127.970	256.453




Schematic – CDAC

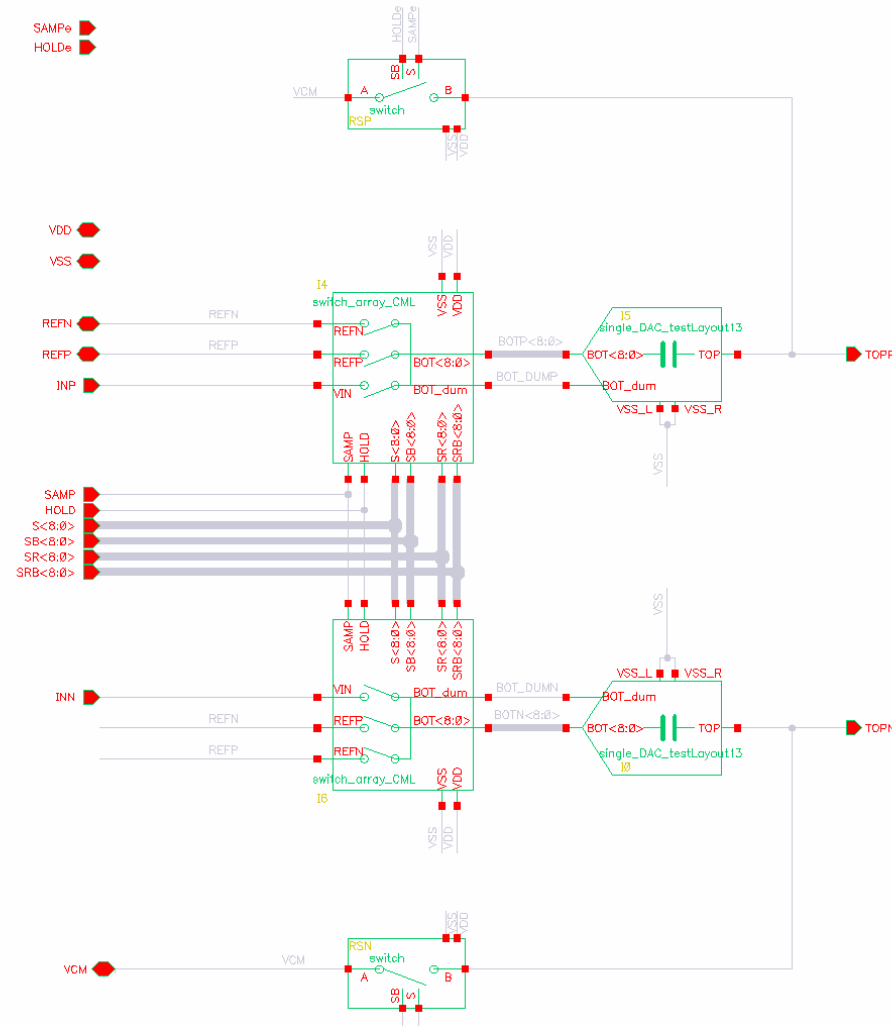




Final Layout – CDAC

 




Schematic – SAR ADC

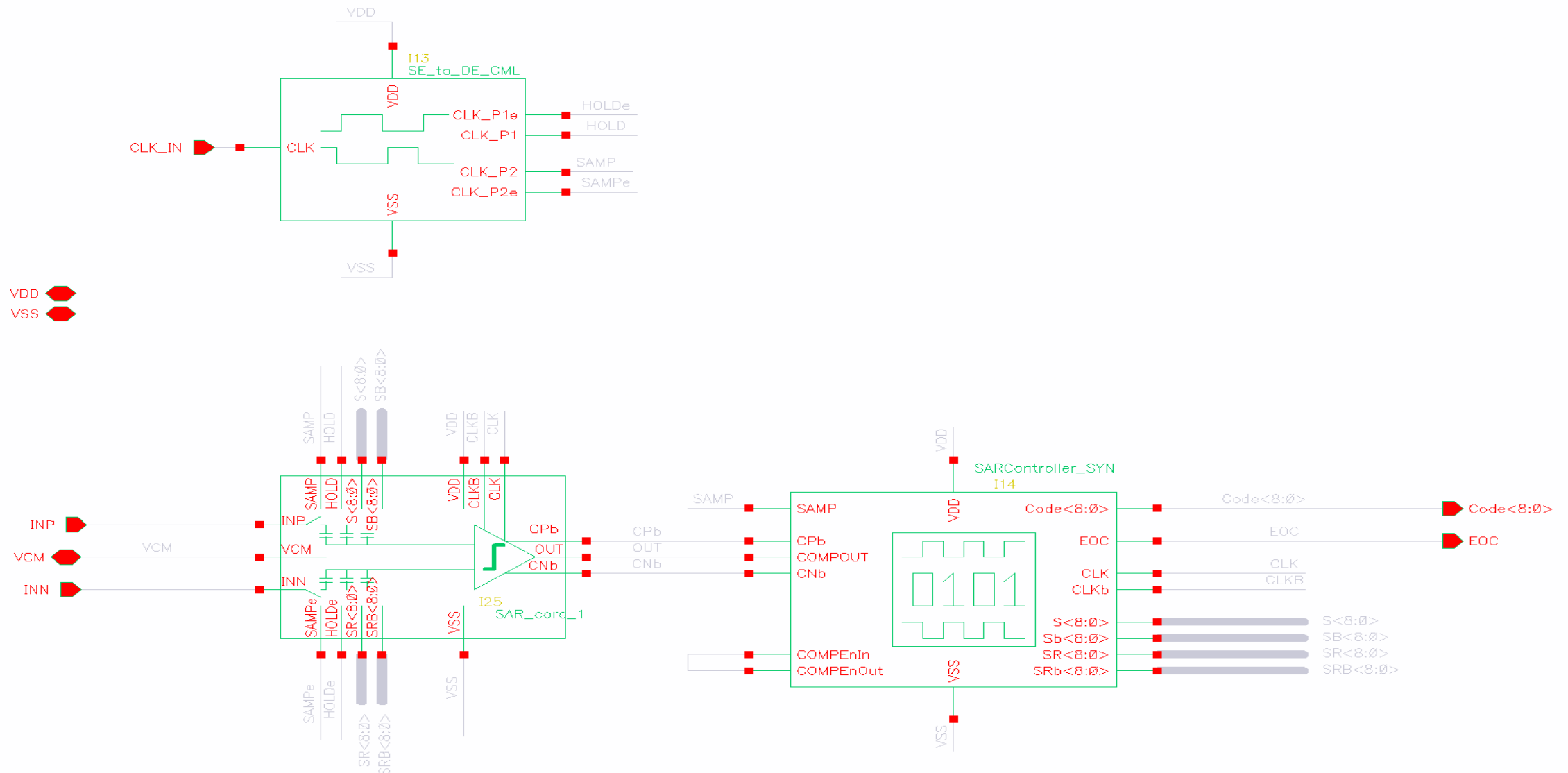



Final Layout – SAR-ADC

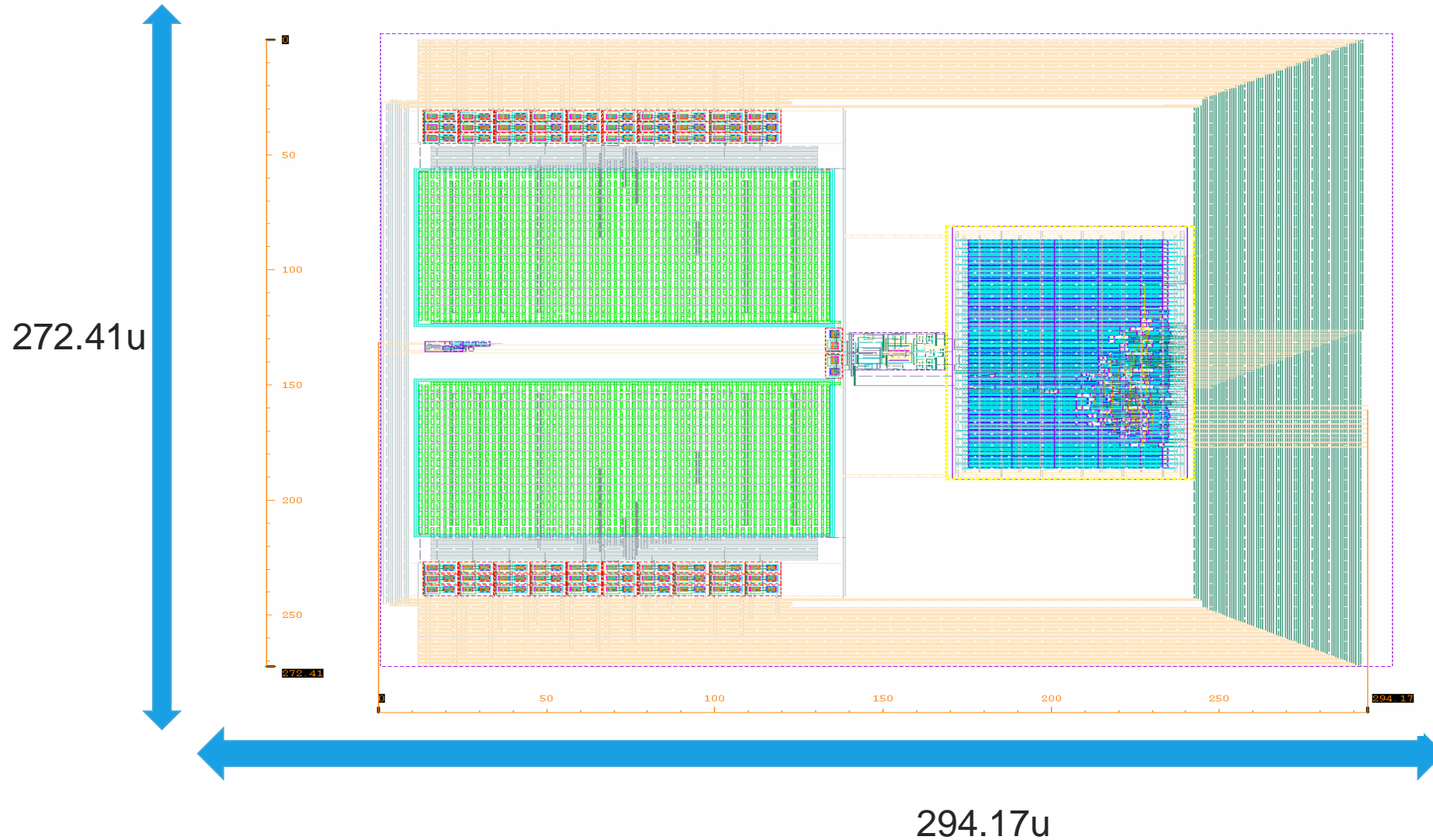



The figure displays four plots related to the simulation of a 2024 circuit, comparing linear and Hamming models.

- Top Left Plot:** Time-domain plot showing the output voltage (V) versus time (us). The y-axis ranges from 0.0 to 550.0 V, and the x-axis ranges from 0.0 to 55.0 us. The plot shows a high-frequency oscillation between approximately 0 V and 550 V.
- Top Right Plot:** Frequency-domain plot showing the output power (dB) versus frequency (MHz). The y-axis ranges from -70.0 to 50.0 dB, and the x-axis ranges from 0.0 to 5.5 MHz. The plot shows a sharp peak at approximately 0.1 MHz, reaching about 40 dB.
- Bottom Left Plot:** Time-domain plot showing the output voltage (V) versus time (us). The y-axis ranges from 0.0 to 550.0 V, and the x-axis ranges from 0.0 to 55.0 us. The plot shows a high-frequency oscillation between approximately 0 V and 550 V.
- Bottom Right Plot:** Frequency-domain plot showing the output power (dB) versus frequency (MHz). The y-axis ranges from -70.0 to 50.0 dB, and the x-axis ranges from 0.0 to 5.5 MHz. The plot shows a sharp peak at approximately 0.1 MHz, reaching about 40 dB.